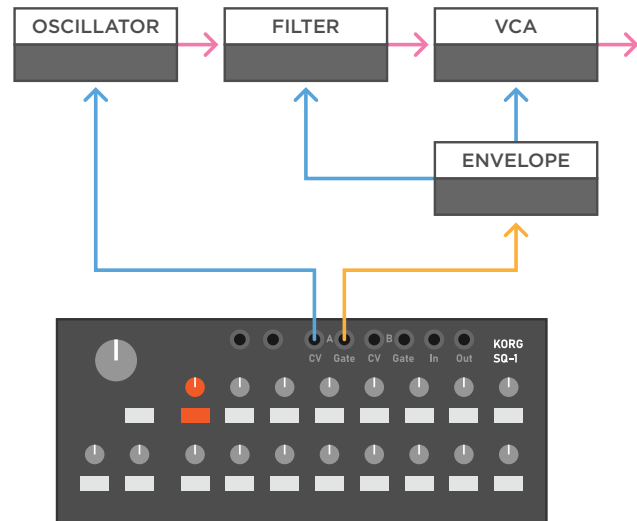


Simple Sequencers

Patch-tips


- Audio
- Control Voltage
- Trigger / Gate



(a)

a - If we make a simple voice with an oscillator, filter and VCA, we can use the quantized CV output of the Korg SQ-1 directly to the 1v/oct input of the oscillator to create a melodic sequence. The gate output of the corresponding sequence can be used to gate an envelope, so we can give some shape to the filter and volume of the sound.

MONOTRAIL TECH TALK

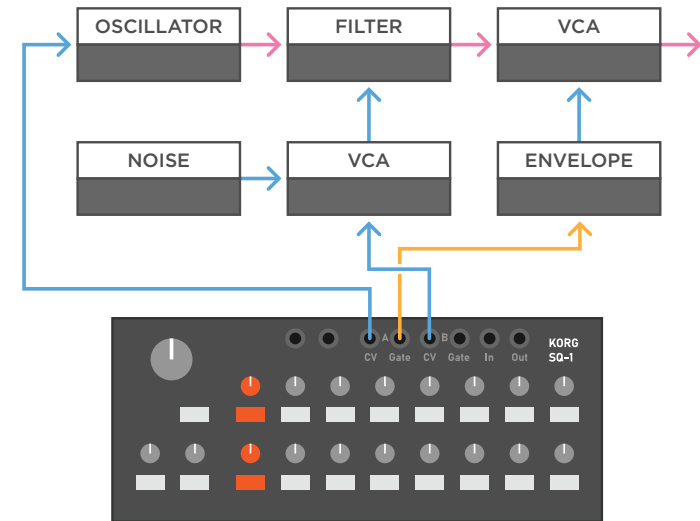


(b)

b - Here the second sequence controls the amount of texture on each step. If you want to create more complex dynamics you can use the second sequencer of the Korg SQ-1 on a VCA to control the amount of modulation between two modules. For example, the amount of modulation from a white noise-source to a filter.

Simple Sequencers

Patch-tips


Audio
Control Voltage
Trigger / Gate

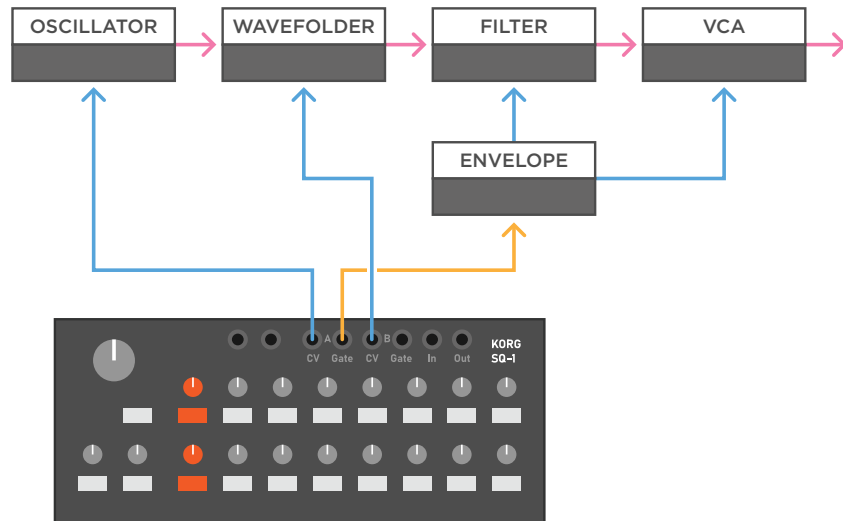

(a)

a - Within a slightly more complex voice, you can use one sequence to control the pitch of the voice and gate the envelope, but experiment with the destination for the second sequence. You can send it to things like a wavefolder, effects module, or filter.

MONOTRAIL TECH TALK

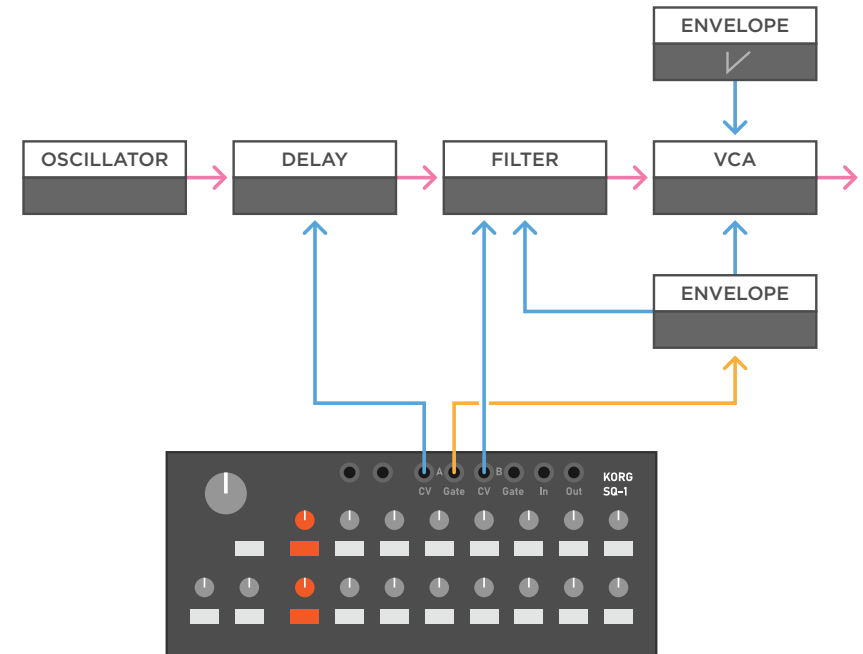

(b)


b - In this patch we use a tuned oscillator to produce a continuous base note. Then run that through a delay module, filter and VCA, with a simple envelope to shape the filter and VCA, resulting in a steady baseline. Then there is some side chain from a steady kick to the VCA, and we use both sequences to make the patch come alive. In this case we use it on the delay time and filter cutoff.

Simple Sequencers

Patch-tips

MONOTRAIL TECH TALK

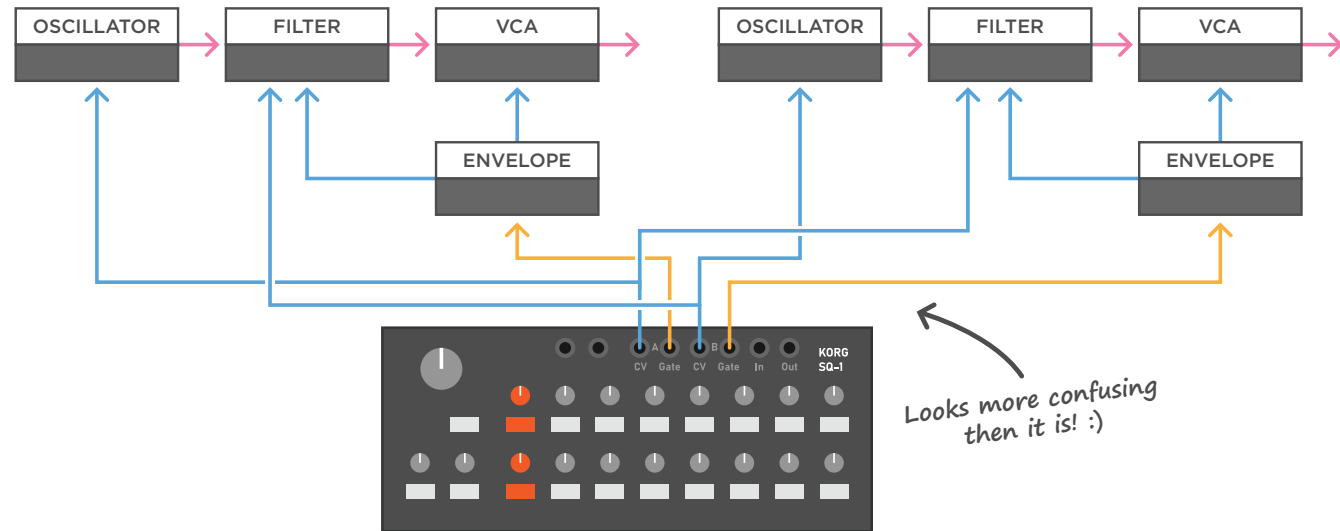- Audio
- Control Voltage
- Trigger / Gate



(a)


a - The SQ-1 can be set to output two independent sequences up to 8 steps. So, if we make two simple voices, we can use the CV and gate outputs to control each voice completely independently

A nice trick with this setup is to multiply each of the 1v/oct signals and use those as CV sequences to parameters in the voices. You could use each of them on their own voice, but you can also use the multiplied signal of each voice, on a parameter of the other, for example, on a parameter of the other filter. This works especially great if you use sequences with different lengths.

Simple Sequencers

Patch-tips

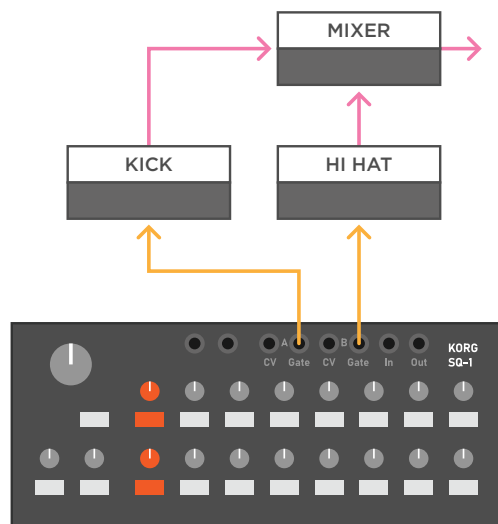
- Audio
- Control Voltage
- Trigger / Gate



(a)

a - You can use the SQ-1 as a simple single 16, or dual 8 step trigger sequencer to trigger things like drum modules. For example, a kick and a snare drum. You have two independent sequences with polyrhythmic possibilities, and they are pretty playable, so it works well to improvise with patterns on the fly.

MONOTRAIL TECH TALK

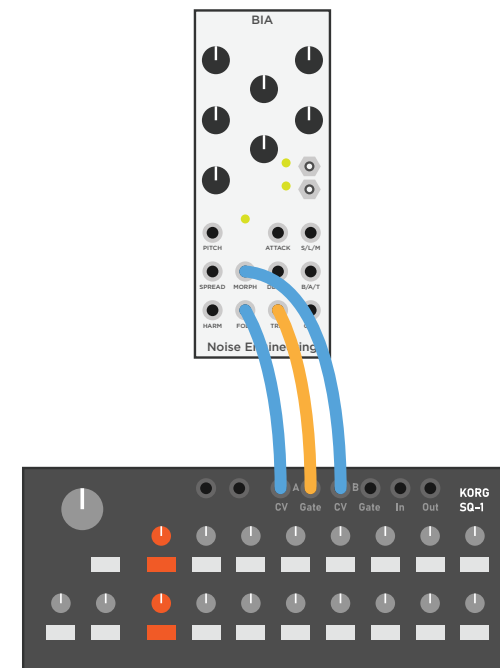


(b)

b - If you have a drum module with more interesting parameters to send control voltages, you can use both the trigger and CV outputs. For example, here I'm using the gate output from the first 8 step sequence to trigger the Noise Engineering Basimilus Iteritas Alter. But I also use the CV output of that first sequence to control the fold, and the second CV output to control the morph.

Simple Sequencers

Patch-tips

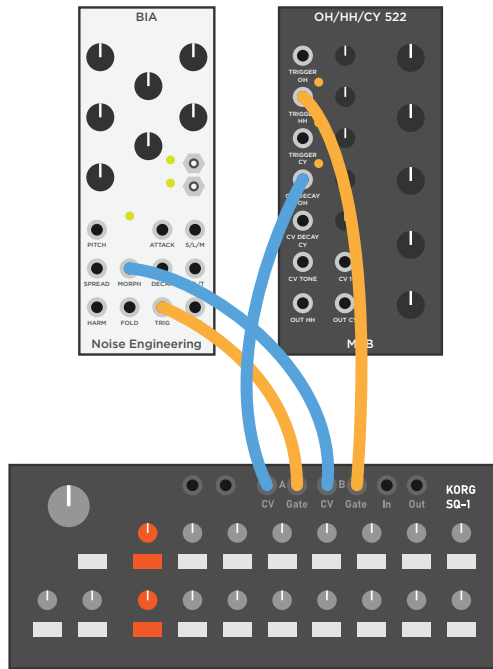— Audio
— Control Voltage
— Trigger / Gate




(a)

a - You can use the trigger sequences of each part to trigger a module, but use the CV sequence of each part to modulate a parameter on the other drum voice for dual dynamic polyrhythms. In this case we use the Basimilus Iteritas Alter and the MFB hi-hat module.

MONOTRAIL

TECH TALK

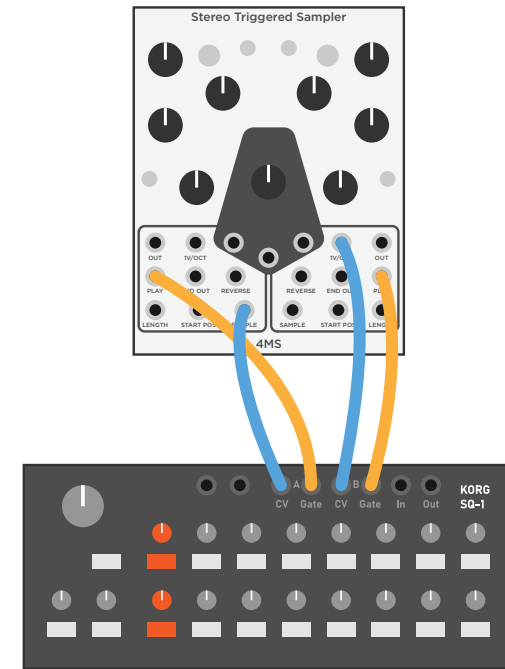


(b)

b - The Korg SQ-1 is also powerful in combination with a sample player. Here we use the 4MS Stereo Triggered Sampler as two independent mono sample players. Send the gate output of the first sequencer to trigger a sample on the first sample player & send the CV output to the sample select, in this case selecting one of ten single drum hits. Then use the second sequencer's trigger to play another sample, like a pre-recorded chord, and the CV output to the 1v/oct input for tuning.

Simple Sequencers

Clock


Audio
Control Voltage
Trigger / Gate

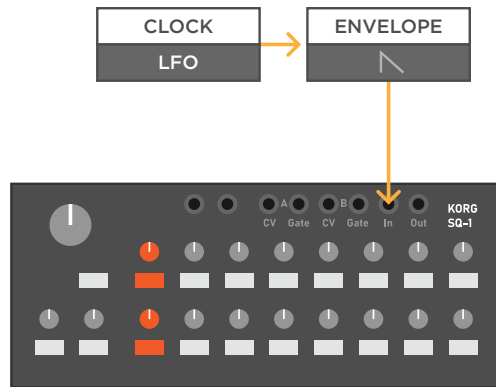

(a)

a - The SQ-1 works really well as a trigger or master clock source. But If you like to sync the SQ-1 to a modular clock, it works best if you use your modular clock, like a square wave LFO, to first trigger an attack decay envelope with a fast attack and a slightly longer decay. Then send that to the sync input of the SQ-1, as it has the tendency to respond to gate-off signals as well.

MONOTRAIL TECH TALK

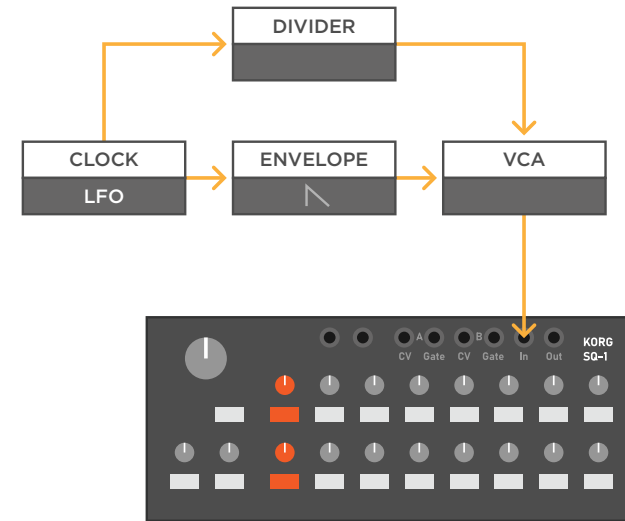

(b)

b - If you like to have start/stop functionality over the SQ-1 from the modular, you can send your modular clock driven envelope through a VCA first. This way you can open that VCA, for example with a clock divider with a slower division, to have the SQ-1 start and stop.